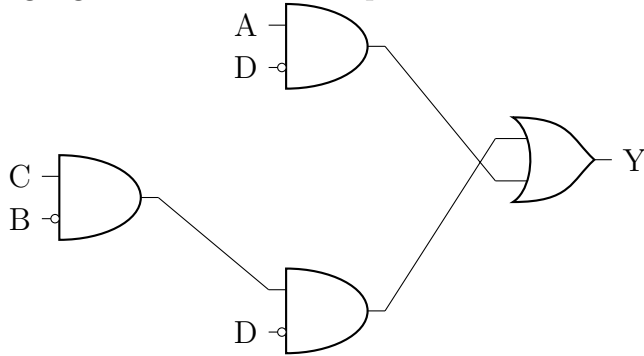# logicgate

V SASHANK REDDY[*]

January 4, 2021

logic gate for e with the expression e=B'CD'+D'A

_____

[*]ggv sir